
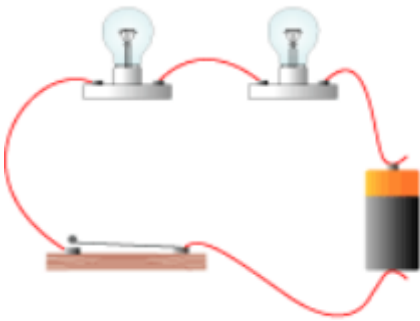
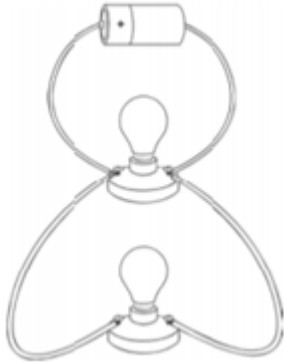


Science activity -drawing circuits

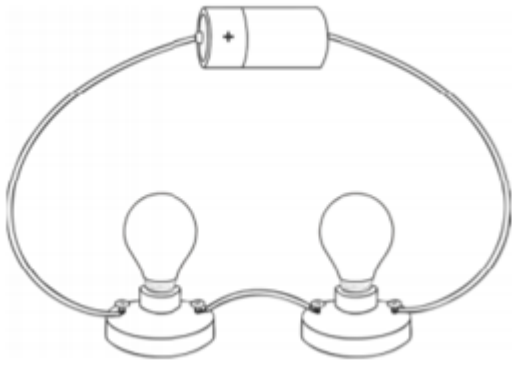

Draw a working circuit that
includes:
lamp, battery, switch and a
buzzer.

Use these symbols to help you


lamp



motor



battery

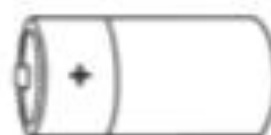







switch



buzzer



Answers

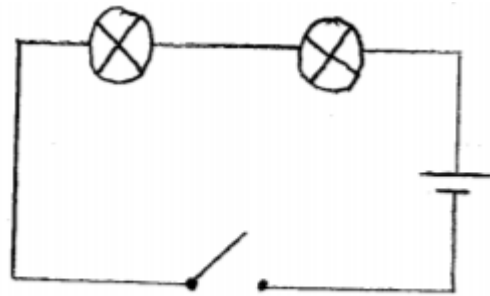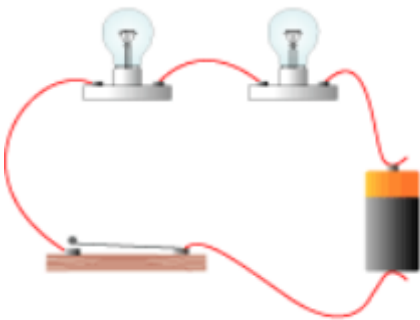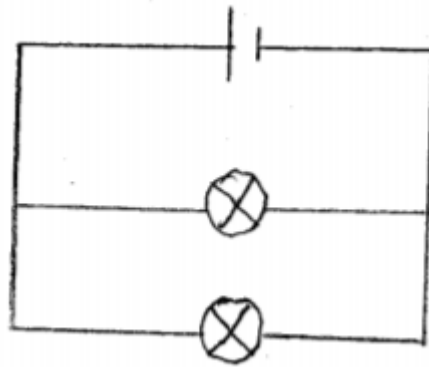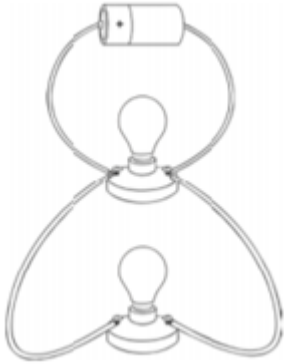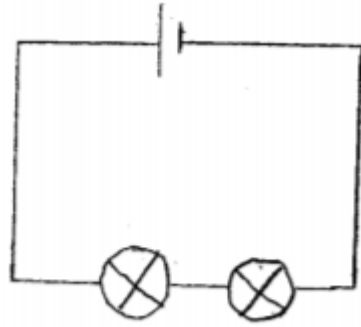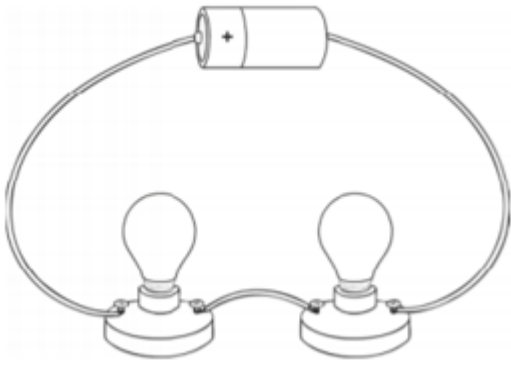

Draw a working circuit that includes:
lamp, battery, switch and a
buzzer.

